

12V DC to 220V AC Converter [Tested Circuit]

January 21, 2016 By Administrator

Inverters are often needed at places where it is not possible to get AC supply from the Mains. An inverter circuit is used to convert the DC power to AC power. **Inverters** can be of two types True/pure sine wave inverters and quasi or modified inverters. These true /pure sine wave inverters are costly ,while modified or quasi inverters are inexpensive.

These modified inverters produce a square wave and these are not used to power delicate electronic equipments . Here, a simple voltage driven inverter circuit using power transistors as switching devices is build, which converts 12V DC signal to single phase 220V AC.

Outline

Principle Behind this Circuit

Inverter circuit Using Transistors

Circuit Diagram

Components required

Working

Output Video

12v DC to 220v AC Converter Circuit Using Astable Multivibrator

Circuit Design Explanation

12v DC to 220v AC Converter Circuit Operation

Applications of 12v DC to 220v AC Converter Circuit


Limitations

Principle Behind this Circuit

The basic idea behind every inverter circuit is to produce oscillations using the given DC and apply these oscillations across the primary of the transformer by amplifying the current. This primary voltage is then stepped up to a higher voltage depending upon the number of turns in primary and secondary coils.

Also get an idea about [12V to 24V DC Converter Circuit](#)



Inverter circuit Using Transistors

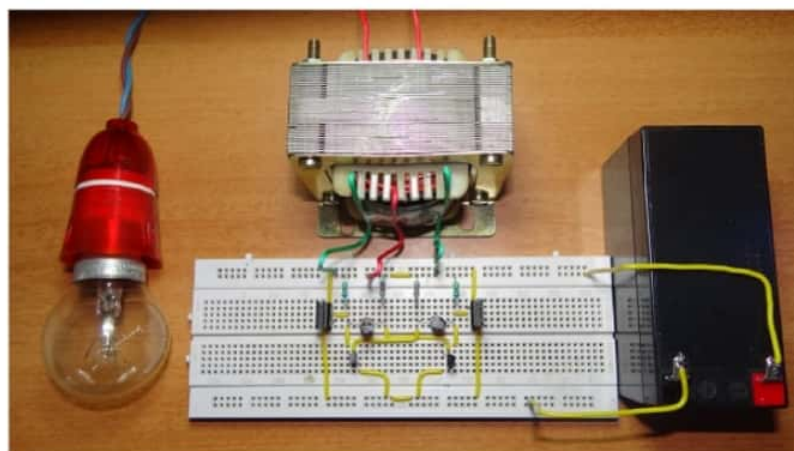

A 12V DC to 220 V AC converter can also be designed using simple transistors. It can be used to power lamps up to **35W** but can be made to drive more powerful loads by adding more MOSFETS.

The inverter implemented in this circuit is a square wave inverter and works with devices that do not require pure sine wave AC.

Circuit Diagram

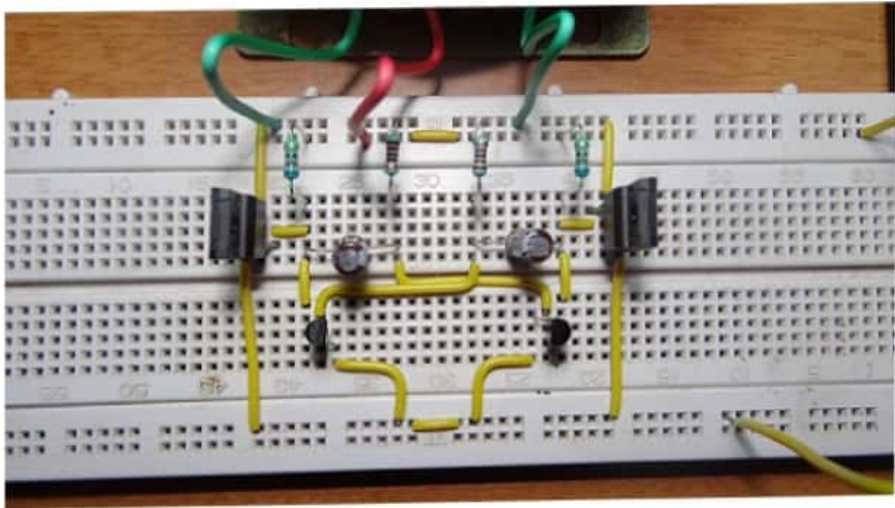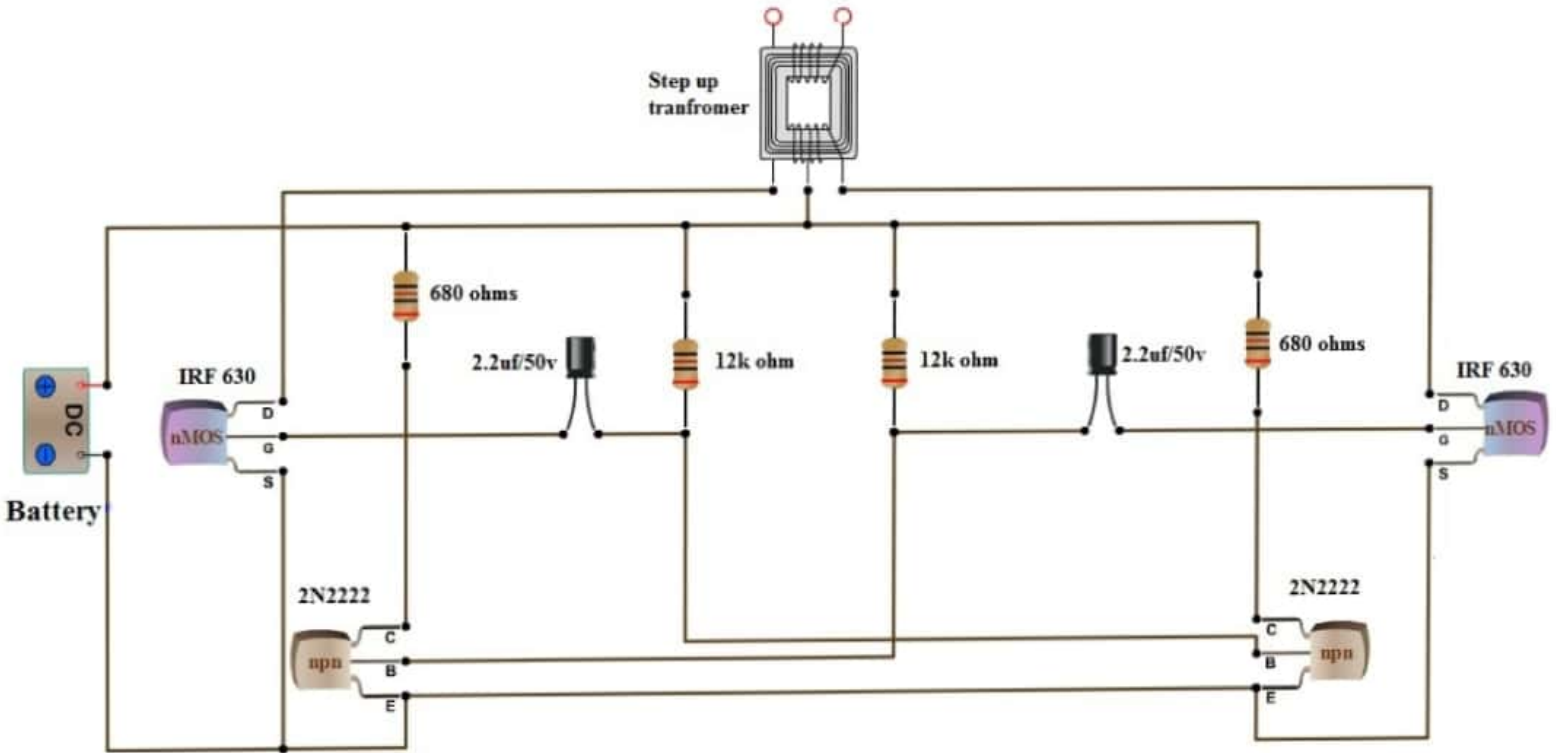

Components required

- 12v Battery
- MOSFET IRF 630 -2
- 2N2222 Transistors
- 2.2uf capacitors-2
- Resistor
 - 680 ohm-2
 - 12k-2
- 12v-220v center tapped step up transformer.
- [2N2222 Datasheet](#)
- [IRF630 Datasheet](#)

Working

The circuit can be divided into three parts: oscillator, amplifier and transformer. A 50Hz oscillator is required as the frequency of AC supply is 50Hz.

This can be achieved by constructing an Astable multivibrator which produces a square wave at 50Hz. In the circuit, R1, R2, R3, R4, C1, C2, T2 and T3 form the oscillator.

Each transistor produces inverting square waves. The values of R1, R2 and C1 (R4, R3 and C2 are identical) will decide the frequency. The formula for the frequency of square wave generated by the astable multivibrator is

$$F = 1/(1.38 \cdot R2 \cdot C1)$$

The inverting signals from the oscillator are amplified by the Power MOSFETS T1 and T4. These amplified signals are given to the step-up transformer with its center tap connected to 12V DC.

The turns ratio of the transformer must be 1:19 in order to convert 12V to 220V. The transformer combines both the inverting signals to generate a 220V alternating square wave output.

By using a 24V battery, loads up to 85W can be powered, but the design is inefficient. In order to increase the capacity of the inverter, the number of MOSFETs must be increased.

To design a 100 watt Inverter read [Simple 100 Watt inverter](#)

12v DC to 220v AC Converter Circuit Using Astable Multivibrator

Inverter circuits can either use thyristors as switching devices or transistors. Normally for low and medium power applications, power transistors are used. The reason for using power transistor is they have very low output impedance, allowing maximum current to flow at the output.

One of the important applications of a transistor is in switching. For this application, the transistor is biased in saturation and cut-off region.


When the transistor is biased in saturation region, both the collector emitter and collector base junctions are forward biased. Here the collector emitter voltage is minimum and collector current is maximum.

Another important aspect of this circuit is the oscillator. An important use of 555 Timer IC is in its use as an astable multivibrator.

An astable multivibrator produces an output signal which switches between the two states and hence can be used as an oscillator. The frequency of oscillation is determined by the values of capacitor and resistors.

[Also Read: [How To Make an Adjustable Timer](#)]

Circuit Diagram

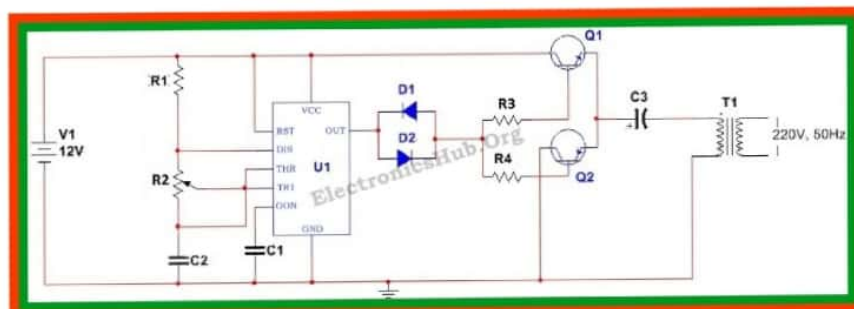

Circuit Diagram of 12v DC to 220v AC Converter - [ElectronicsHub.Org](#)

Circuit Components

- V1 = 12V
- R1 = 10K
- R2 = 150K
- R3 = 10Ohms
- R4 = 10Ohms
- Q1 = TIP41
- Q2 = TIP42
- D1 = D2 = 1N4007
- C3 = 2200uF
- T1 = 12V/220V step up transformer

Circuit Design Explanation

Circuit Design Explanation

Oscillator Design: An astable multivibrator can be used as an oscillator. Here an astable multivibrator using 555 timer is designed. We know, frequency of oscillations for a 555 timer in astable mode is given by:

$$f = 1.44 / (R1 + 2 \cdot R2) \cdot C$$

where R1 is the resistance between discharge pin and Vcc, R2 is the resistance between discharge pin and threshold pin and C is capacitance between threshold pin and ground. Also the duty cycle of the output signal is given by:

$$D = (R1 + R2) / (R1 + 2 \cdot R2)$$

Since our requirement is $f = 50\text{Hz}$ and $D = 50\%$ and assuming C to be $0.1\mu\text{F}$, we can calculate the values of R1 and R2 to be 10K and 140K Ohms respectively. Here we prefer using a 150K potentiometer to fine tune the output signal.

Also a ceramic capacitor of $0.01\mu\text{F}$ is used between the control pin and ground.

Switching Circuit Design: Our main aim is to develop an AC signal of 220V . This requires use of high power transistors to allow the flow of maximum amount of current to the load. For this reason we use a power transistor TIP41 with a maximum collector current of 6A , where the base current is given by the collector current divided by the DC current gain. This gives a bias current of about $0.4\text{A} \cdot 10$, i.e. 4A . However since this current is more than the maximum base current of the transistor, we prefer a value less than the maximum base current. Let us assume the bias current to be 1A . The bias resistor is then given by

$$R_b = (V_{cc} - V_{BE(ON)}) / I_{bias}$$

For each transistor, the $V_{BE(ON)}$ is about 2V . Thus R_b for each is calculated to be 10 Ohms . Since the diodes are used for biasing, the forward voltage drop across the diodes should be equal to the forward voltage drops across the transistors. For this reason, diodes 1N4007 are used.

The design considerations for both the PNP and NPN transistors are same. We are using a PNP power transistor TIP42.

Output Load Design: Since the output from the switching circuit is a pulse width modulated output, it might contain harmonic frequencies other than the fundamental AC frequency. For this reason, an electrolyte capacitor needs to be used to allow only the fundamental frequency to pass through it. Here we use an electrolyte capacitor of $2200\mu\text{F}$, large enough to filter out the harmonics. Since it is required to get 220V output, it is preferred to use a step up transformer. Here a $12\text{V}/220\text{V}$ step up transformer is used.

12v DC to 220v AC Converter Circuit Operation

- When this device is powered using the 12V battery, the 555 timer connected in astable mode produces square wave signal of 50Hz frequency.
- When the output is at logic high level, diode D2 will conduct and the current will pass through diode D1, R3 to the base of transistor Q1.
- Thus transistor Q1 will be switched on. When the output is at logic low level, diode D1 will conduct and current will flow via and D1 and R4 to the base of Q2, causing it to be switched on.
- This allows the DC voltage to be produced across the primary of the transformer at alternate intervals. The capacitor ensures that the frequency of the signal is at the required fundamental frequency.
- This 12V AC signal across the primary of the transformer is then stepped up to 220V AC signal across the transformer secondary.

Applications of 12v DC to 220v AC Converter Circuit

1. This circuit can be used in cars and other vehicles to charge small batteries.
2. This circuit can be used to drive low power AC motors
3. It can be used in solar power system.

Limitations

1. Since 555 timer is used, the frequency of oscillation is limited to 50Hz .