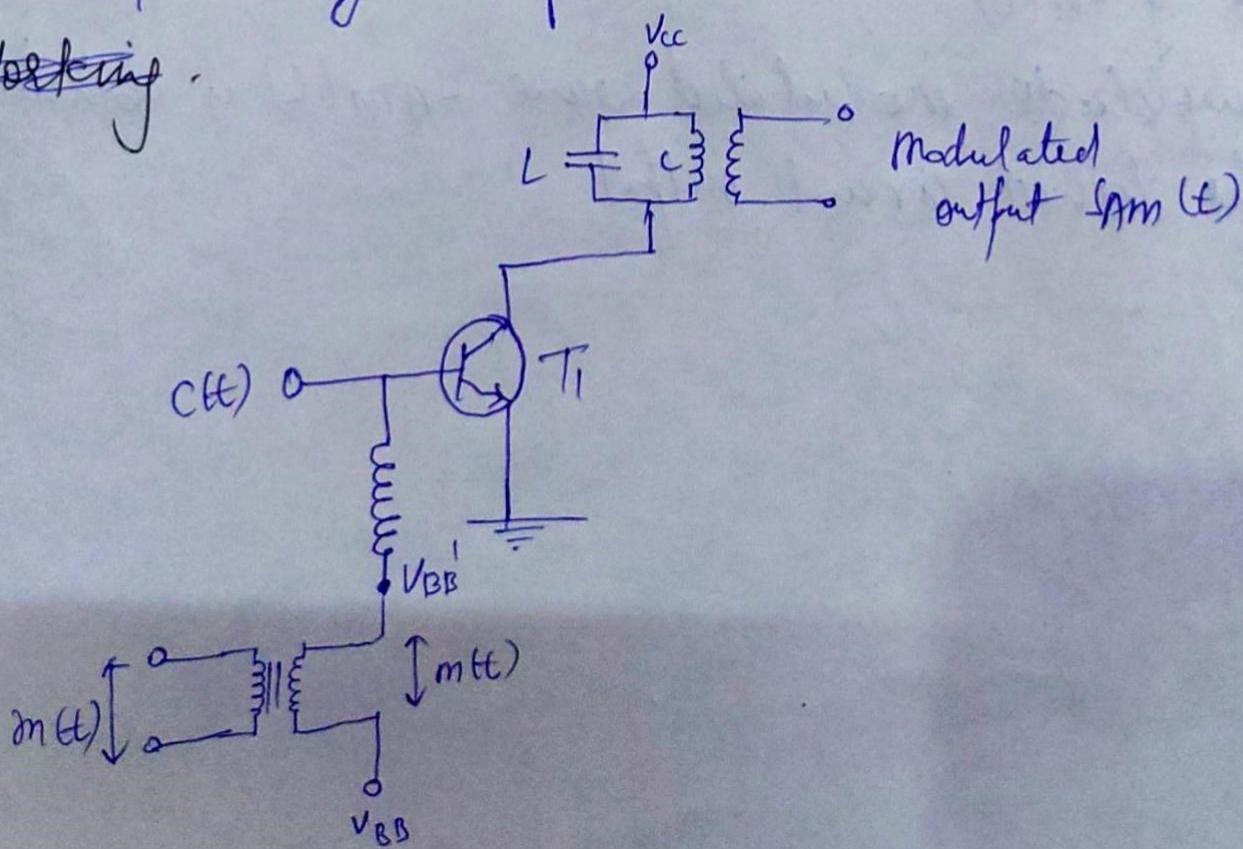


## ② Base Modulator

- Low-level AM modulation technique.
- The carrier and the modulating signal are applied to the base region of the BJT, hence it is called base modulator.
- Carrier is applied to the base of the transistor  $T_1$ .
- Modulating signal is applied in series to the base-biasing voltage ( $V_{BB}$ )
- The collector terminal of the transistor is connected to a tuned ~~RLC~~ LC circuit, to select the frequency of the output.
- ~~RF~~ Radio frequency coil (RFC) is used to stop the high frequency carrier signal from reaching to the audio-frequency transformer.

→ Working.



## Working :

- Message signal is amplified using the audio-frequency transformer, and appears at the secondary winding of the transformer.
- $V_{BB}$  and  $m(t)$  appear in series and so they get added or subtracted depending upon the amplitude,  
(added if AM is +ve, subtracted if AM is -ve)
- The supply current at  $T_1$
- The base-bias voltage  $V_{B1} = V_{BB} + m(t)$ . and thus the amplitude of the base-bias voltage will vary according to the amplitude of  $m(t)$ .
- Due to this, the output at the collector of the BJT will also start changing according to the amplitude of  $m(t)$ .
- The amplitude modulated wave  $s_{Am(t)}$  is obtained at the tuned circuit output.